# 11. 논리제어



#### **Contents**

- Introduction to logic control
- PLC (Programmable Logic Controller)
- **♦** Ladder logic



## Introduction to logic control (1)

### Two types of control

- Motion control (CNC & Industrial robots)
- Logic (discrete) control

#### **♦** What is discrete control?

- Deal with parameters that change at discrete moments
- Discrete: Binary or 1/0 or True/False
- Example
  - Limit switch: contact/no contact
  - Motor: on/off
  - Valve: closed/open



## Introduction to logic control (2)

### ◆ Two category of discrete control


- Logic control: event-driven changes in the system
- Sequence control: time-driven changes in the system


### Characteristics of logic control


- No memory (does not consider any previous values of input)
- Time-independent
- Basic elements (logic gates): AND, OR, NOT



## Logic gates: AND, OR, NOT

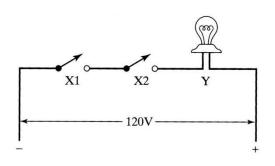

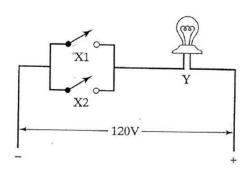

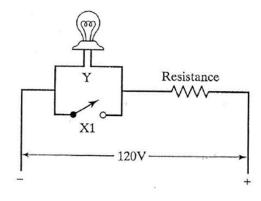


AND



| A — |  |
|-----|--|
| в   |  |

OR

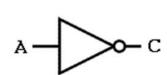


NOT


| Inputs |   | Output |
|--------|---|--------|
| A      | В | C      |
| 0      | 0 | 0      |
| 0      | 1 | 0      |
| 1      | 0 | 0      |
| 1      | 1 | 1      |

| Inputs |   | Output |
|--------|---|--------|
| A      | В | C      |
| 0      | 0 | 0      |
| 0      | 1 | 1      |
| 1      | 0 | 1      |
| 1      | 1 | 1      |

| Input | Output |
|-------|--------|
| A     | C      |
| 0     | 1      |
| 1     | 0      |

## Logic gates: NAND, NOR, XOR

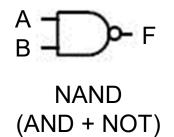

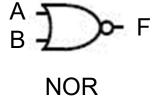

(OR + NOT)


| Α | В | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


| Α | В | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

| Α | В | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

## Logic gates

### Push button switch example

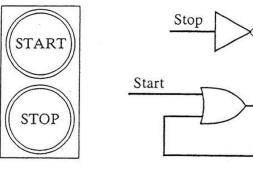

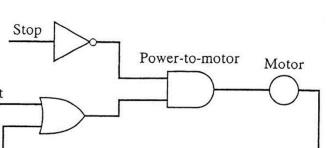

#### Truth table

| Start | Stop | Motor | Power-to-<br>motor |
|-------|------|-------|--------------------|
| 0     | 0    | 0     | 0                  |
| 0     | 1    | 0     | 0                  |
| 1     | 0    | 0     | 1                  |
| 1     | 1    | 0     | 0                  |
| 0     | 0    | 1     | 1                  |
| 0     | 1    | 1     | 0                  |
| 1     | 0    | 1     | 1                  |
| 1     | 1    | 1     | 0                  |


## PLC (Programmable Logic Controller) (1)

#### What is PLC?

- A microprocessor-based device to replace wiring and relay for logic control
- Programming is easier than wiring!
- Advantages of PLC
  - Smaller than relay logic network
  - Better reliability
  - Better connectivity to computer system
  - Variety of control functions
    - ✓ Timer, counter, ...


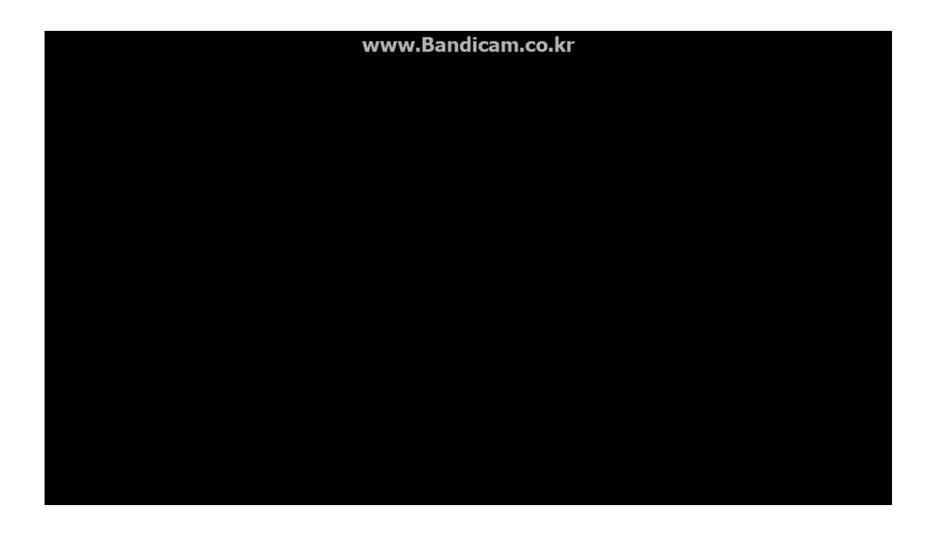
## PLC (Programmable Logic Controller) (1)






## PLC (Programmable Logic Controller) (2)
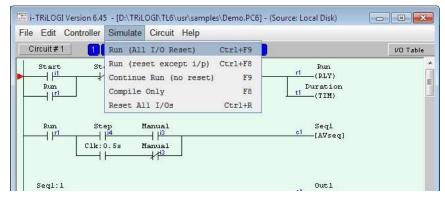
### Components of PLC

- Processor
- Memory
- I/O
- Programming device



Screen for PLC programming





**Commercial PLCs** 



## PLC (Programmable Logic Controller) (3)


- Standard logic programming languages (IEC 61131-3)
  - The third part (of 8) of the open international standard
    IEC 61131 for programmable logic controllers
    - Ladder diagram (LD), graphical
    - Function block diagram (FBD), graphical
    - Sequential function chart (SFC), graphical
    - Continuous Function Chart (CFC), graphical
    - Structured text (ST), textual
    - Instruction list (IL), textual



## Ladder logic (1)
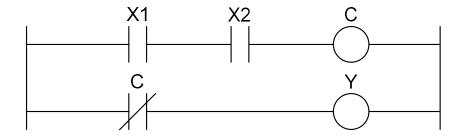
#### Ladder Logic Diagram


- Programming language that represents a program by a graphical diagram based on the circuit diagrams of relay logic hardware
- Used to develop software for programmable logic controller (PLC) used in industrial control applications
  - PLC: used to configure complex automation systems






## Ladder logic (2)

### Symbol for ladder logic diagram

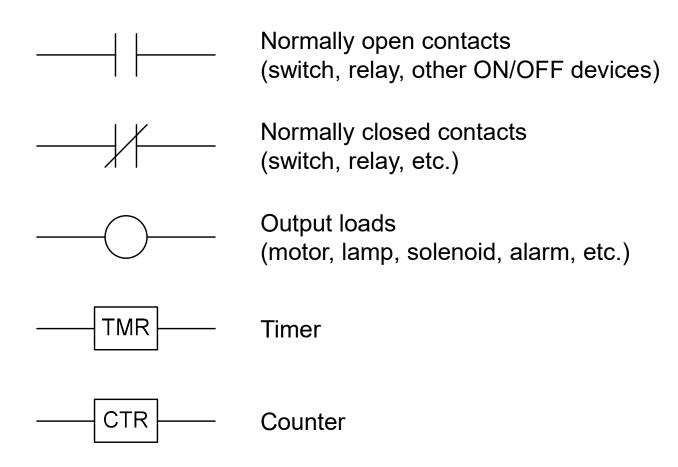



## Ladder logic (3)

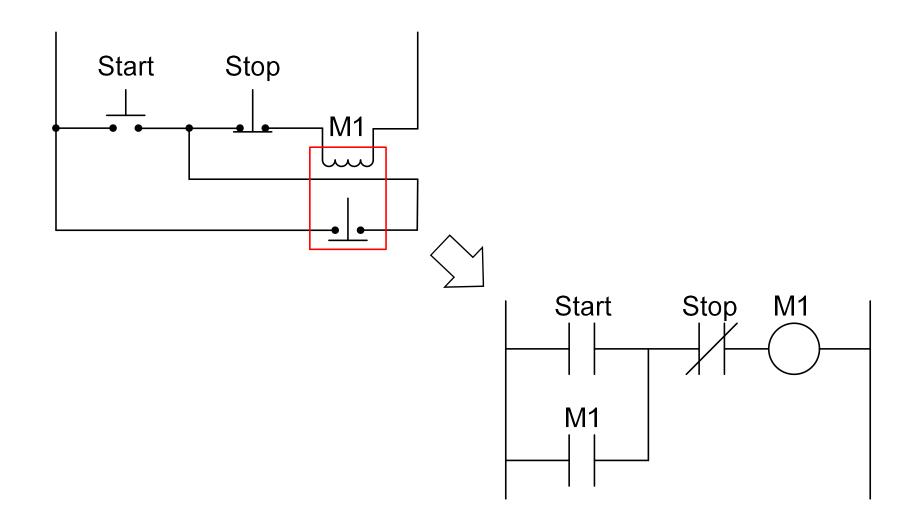





## Ladder logic (4)

#### **◆** AND, OR, NOT in ladder logic

- AND
  - Y = X1 AND X2

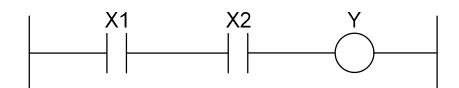

- OR
  - Y = X1 OR X2

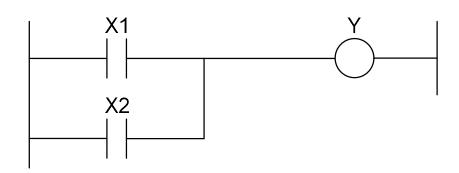


- NOT
  - Y = NOT X1



## Ladder logic (5)


### **♦** Control relay

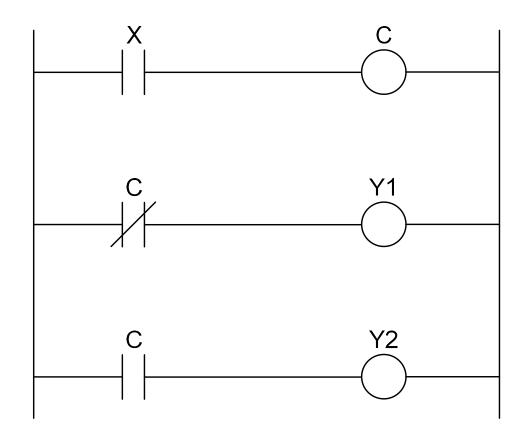



## Ladder logic (6)
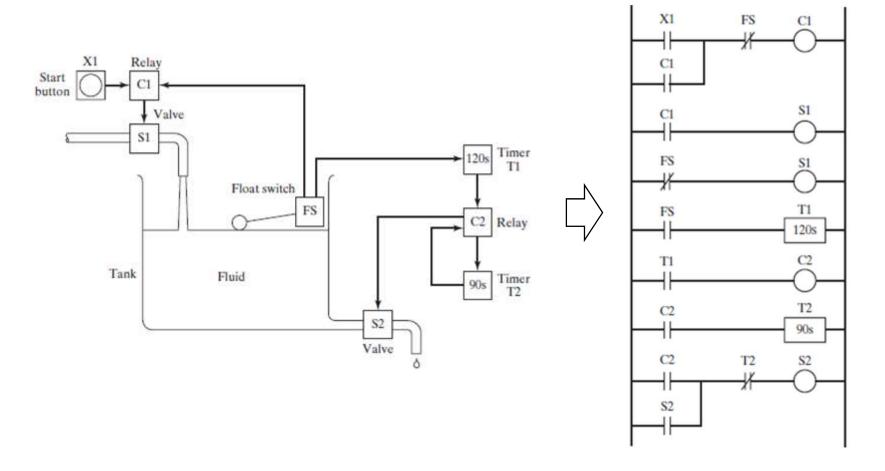
### **♦** Fluid filling operation example





## Ladder logic (7)

#### Example 1

Draw ladder logic diagram to configure automatic

